

Homework


- Reading
 - Tokheim, Chapter 12-1 through 12-4
- Machine Projects
 - MP4 due at start of next class
- Labs
 - Continue with your assigned section

Read Only Memory (ROM)

- PC uses it to hold BIOS for system and I/O drivers
- Slow (100-200 nanoseconds)
- Various forms:
 - Read Only Memory (ROM)
 - Programmable Read Only Memory (PROM)
 - Erasable Programmable Read Only Memory (EPROM)
 - Electrically Erasable Programmable ROM (EEPROM)
 - Flash memory

Read Only Memory (ROM)


- Diode Matrix Design

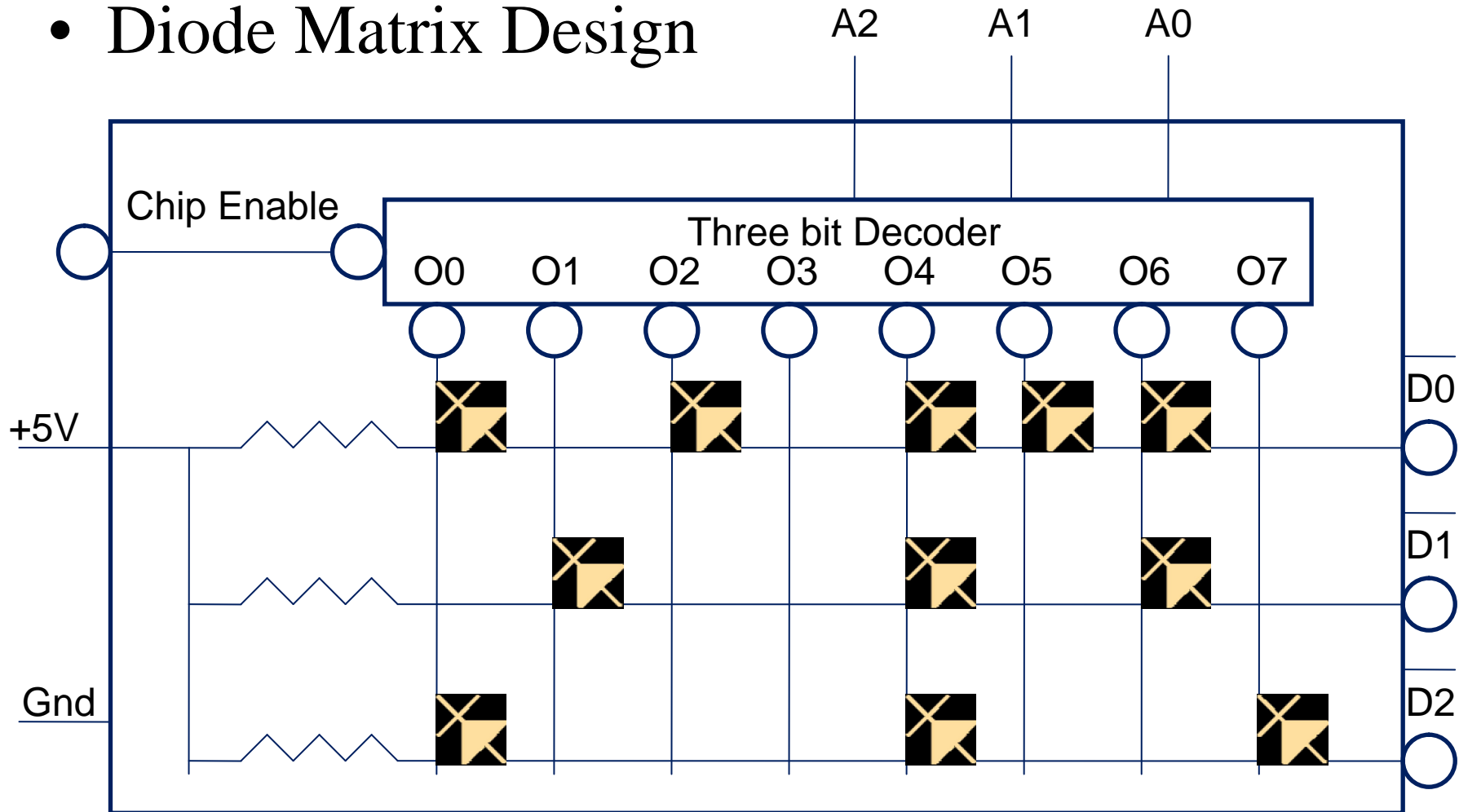

Presence of a diode means a 1, absence of a diode = 0

Programmable ROM


- Diode Matrix Design

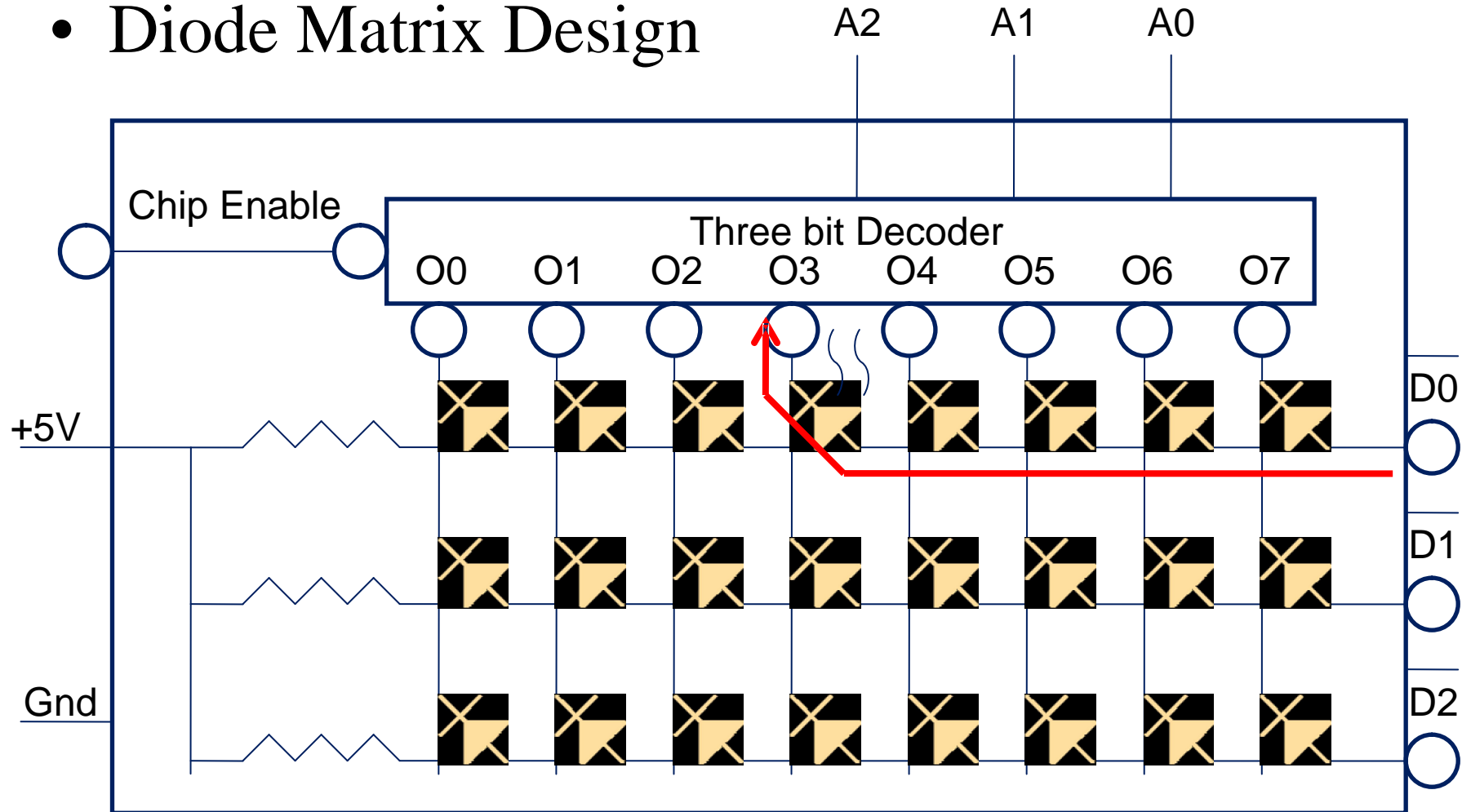

Starts with all diodes/all ones. Burn out diodes where value needs to be zero. ⁴

Random Access Memory (RAM)

 
- Static RAM = an array of full flip-flops
- Simple interface and fast (10-20 nsec) but more costly (2 - 4X) than ROM



- Small capacity compared to Dynamic RAMs

Dynamic RAM (DRAM)

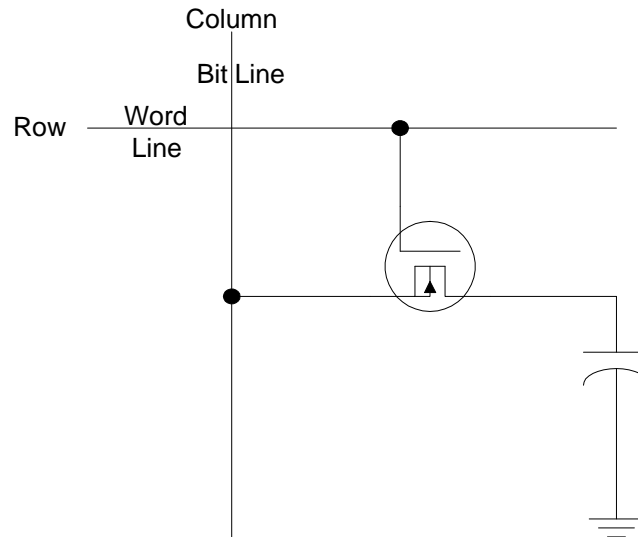- Square array of simple one transistor memory cells
- Capacitance at input to transistor remembers a 0 or 1



- Reading contents of the cell is destructive
- Over time, the charge leaks away (in milliseconds)

Dynamic RAM (DRAM)

- For both reasons, HW must perform a *memory refresh*
- Regularly reading/writing on a row and column basis
- Advantages are:
 - Cells are simple
 - Uses less power
- Disadvantage:
 - Slower (20 - 30 nsec access time)
 - Total cycle time is 2X due to refresh after read
- Bottom line
 - 2-4X less chip area and 2-4X less power
 - Interleaving and access in column or page mode

Example Layouts of Memory Parts

- Organized 1 Meg x 1 or Organized 128K x 8




Number of Data Bit Pins Attached to Data Bus

Full Address Decoding

- Each location within a memory component responds to only one unique address
- Need to use all the address lines in decoding
- May choose not to fill-in some portions of the address space with real memory (empty spots)


Addressing Memory Components

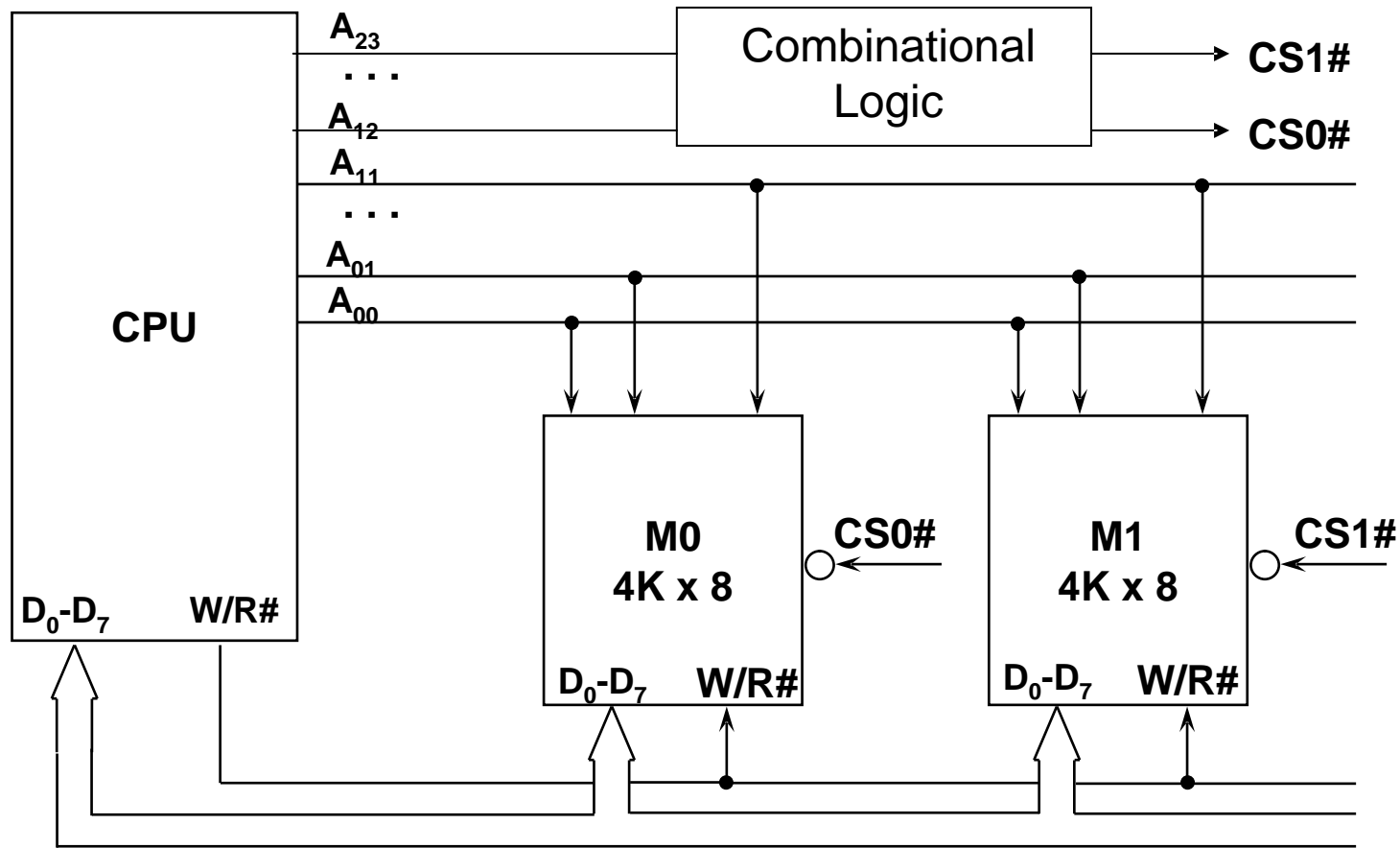


Partial Address Decoding

- Simpler and less expensive
- Some address lines are NOT used in the address decoding process to generate chip enable signals
- Many groups of addresses can map to the same physical memory chip

Partial Address Decoding

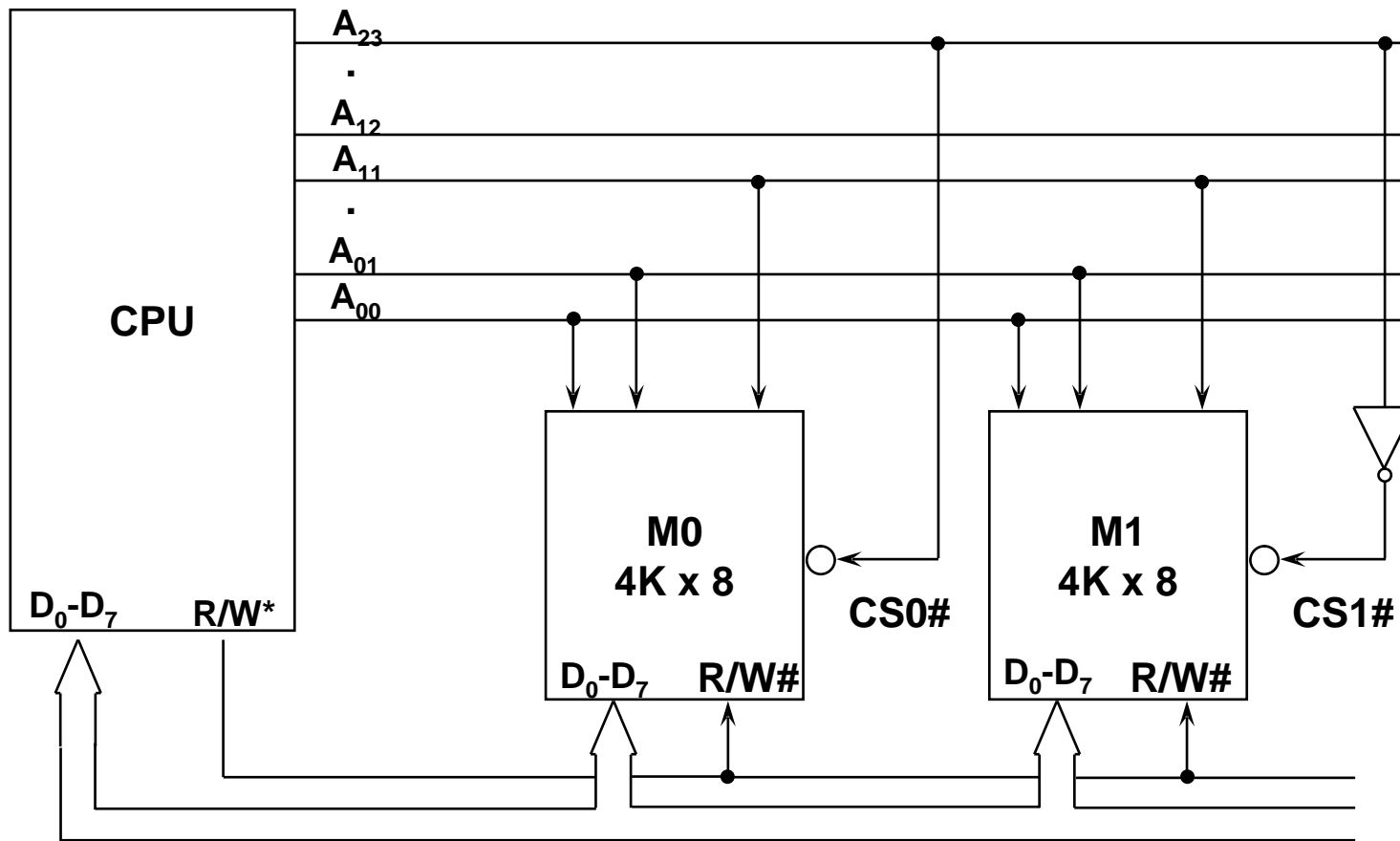

Memory Map for Partial Decoding

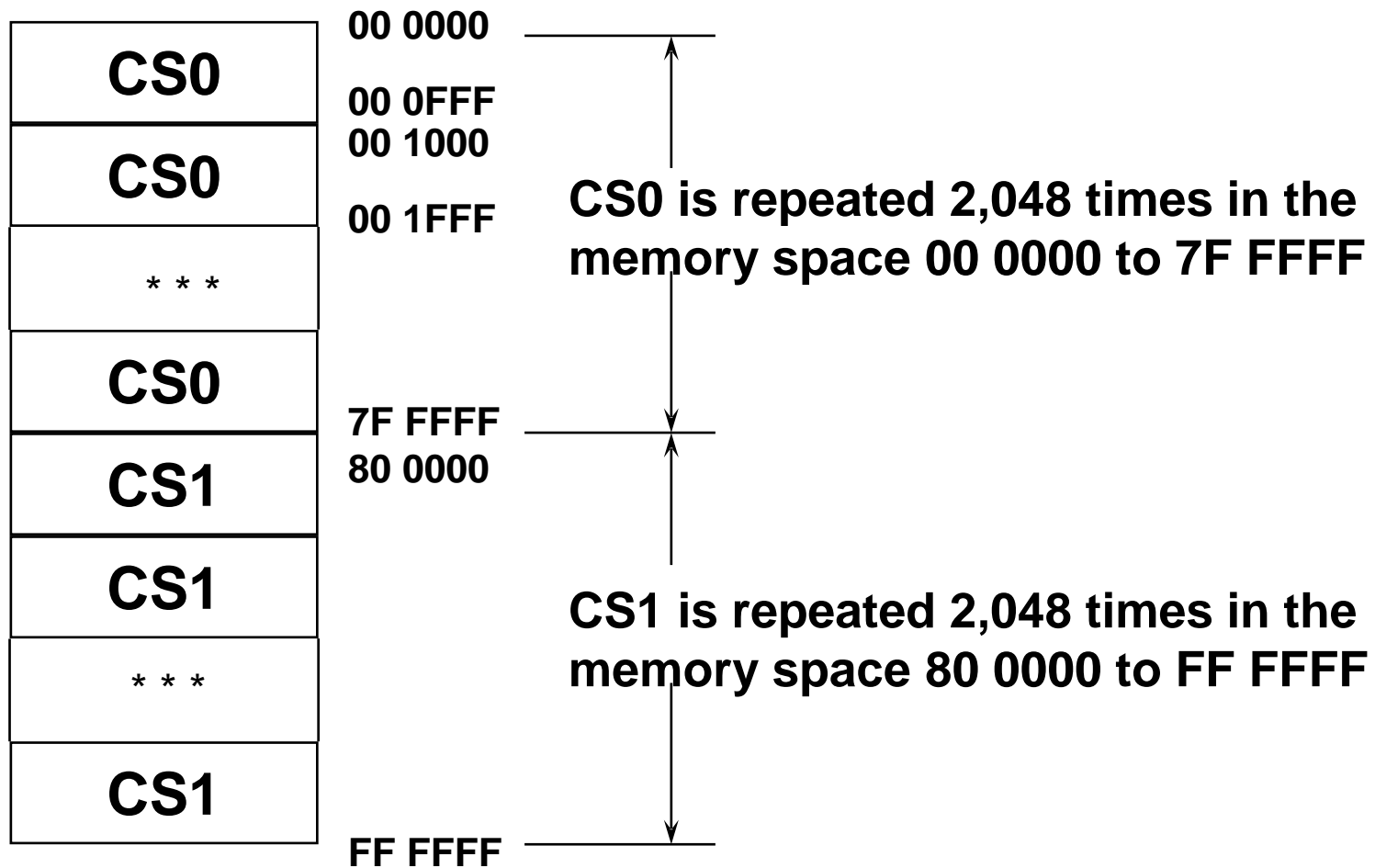


Comb. Logic for CS0 and CS1

CS0	00 0000
CS0	00 0FFF 00 1000
***	00 1FFF
CS0	7F FFFF
CS1	80 0000
CS1	

CS1	FF FFFF

	A23	A22	A21	A20	A19	A18	A17	A16	A15	A14	A13	A12	A11	A10	A09	A08
CS0	0	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X
CS1	1	X	X	X	X	X	X	X	X	X	X	X	X	X	X	X

 


Mixed Address Decoding

- A mixture or a compromise between partial and full address decoding
- Divide the memory space into a number of fully decoded blocks, generally of equal size
- Use high-order address bits to select the block and low-order address bits to select a sub-block

Comb. Logic for CS0, CS1, CS2, & CS3

	A23	A22	A21	A20	A19	A18	A17	A16	A15	A14	A13	A12	A11	A10	A09	A08
CS0	0	0	0	0	0	0	0	0	0	0	0	0	X	X	X	X
CS1	0	1	0	0	0	0	0	0	0	0	0	0	X	X	X	X
CS2	1	X	X	X	X	X	X	X	X	X	X	0	X	X	X	X
CS3	1	X	X	X	X	X	X	X	X	X	X	1	X	X	X	X

 Logic Diagram for CS0# and CS1#
 Similar to Diagram on Slide 11
 Except A_{22} and A_{12} are swapped



Memory Map for Mixed Decoding

