

Boolean Algebra

Boolean algebra provides the operations and the rules for working with the set **{0, 1}**.

These are the rules that underlie **electronic circuits**, and the methods we will discuss are fundamental to **VLSI design**.

We are going to focus on three operations:

- Boolean complementation,
- Boolean sum, and
- Boolean product

24 Nov 2015 CS 320 1

Boolean Operations

The **complement** is denoted by a bar (on the slides, we may use a minus sign). It is defined by $\bar{0} = 1$ and $\bar{1} = 0$ (or $-0 = 1$ and $-1 = 0$)

The **Boolean sum**, denoted by + or by OR, has the following values:
 $1 + 1 = 1, 1 + 0 = 1, 0 + 1 = 1, 0 + 0 = 0$

The **Boolean product**, denoted by \cdot or by AND, has the following values:
 $1 \cdot 1 = 1, 1 \cdot 0 = 0, 0 \cdot 1 = 0, 0 \cdot 0 = 0$

24 Nov 2015 CS 320 2

Boolean Functions and Expressions

Definition: Let $B = \{0, 1\}$. The variable x is called a **Boolean variable** if it assumes values only from B .

A function from B^n , the set $\{(x_1, x_2, \dots, x_n) \mid x_i \in B, 1 \leq i \leq n\}$, to B is called a **Boolean function of degree n** .

Boolean functions can be represented using expressions made up from the variables and Boolean operations.

24 Nov 2015 CS 320 3

Boolean Functions and Expressions

The **Boolean expressions** in the variables x_1, x_2, \dots, x_n are defined recursively as follows:

- 0, 1, x_1, x_2, \dots, x_n are Boolean expressions.
- If E_1 and E_2 are Boolean expressions, then $(\neg E_1)$, $(E_1 E_2)$, and $(E_1 + E_2)$ are Boolean expressions.

Each Boolean expression represents a Boolean function. The values of this function are obtained by substituting 0 and 1 for the variables in the expression.

24 Nov 2015 CS 320 4

Boolean Functions and Expressions

For example, we can create Boolean expression in the variables $x, y,$ and z using the "building blocks" 0, 1, $x, y,$ and $z,$ and the construction rules:

Since x and y are Boolean expressions, so is xy .

Since z is a Boolean expression, so is (\bar{z}) .

Since xy and (\bar{z}) are expressions, so is $xy + (\bar{z})$.

... and so on...

24 Nov 2015 CS 320 5

Boolean Functions and Expressions

Example: Give a Boolean expression for the Boolean function $F(x, y)$ as defined by the following table:

x	y	F(x, y)
0	0	0
0	1	1
1	0	0
1	1	0

Possible solution: $F(x, y) = (\bar{x}) \cdot y$

24 Nov 2015 CS 320 6

Boolean Functions and Expressions

There is a simple method for deriving a Boolean expression for a function that is defined by a table. This method is based on **minterms**.

Definition: A **literal** is a Boolean variable or its complement. A **minterm** of the Boolean variables x_1, x_2, \dots, x_n is a Boolean product $y_1y_2\dots y_n$, where $y_i = x_i$ or $y_i = \bar{x}_i$.

Hence, a minterm is a product of n literals, with one literal for each variable.

24 Nov 2015 CS 320 7

Boolean Functions and Expressions

Definition: The Boolean functions F and G of n variables are **equal** if and only if $F(b_1, b_2, \dots, b_n) = G(b_1, b_2, \dots, b_n)$ whenever b_1, b_2, \dots, b_n belong to B .

Two different Boolean expressions that represent the same function are called **equivalent**.

For example, the Boolean expressions $xy, xy + 0,$ and $xy \cdot 1$ are equivalent.

24 Nov 2015 CS 320 8

Boolean Functions and Expressions

The **complement** of the Boolean function F is the function \bar{F} , where $\bar{F}(b_1, b_2, \dots, b_n) = \overline{F(b_1, b_2, \dots, b_n)}$.

Let F and G be Boolean functions of degree n . The **Boolean sum $F+G$** and **Boolean product FG** are then defined by

$$(F+G)(b_1, b_2, \dots, b_n) = F(b_1, b_2, \dots, b_n) + G(b_1, b_2, \dots, b_n)$$

$$(FG)(b_1, b_2, \dots, b_n) = F(b_1, b_2, \dots, b_n) G(b_1, b_2, \dots, b_n)$$

24 Nov 2015 CS 320 9

Boolean Functions and Expressions

Question: How many different Boolean functions of degree 2 are there?

Solution: There are 16 of them, F_1, F_2, \dots, F_{16} :

x	y	F_1	F_2	F_3	F_4	F_5	F_6	F_7	F_8	F_9	F_{10}	F_{11}	F_{12}	F_{13}	F_{14}	F_{15}	F_{16}
0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1

24 Nov 2015 CS 320 10

Boolean Functions and Expressions

Question: How many different Boolean functions of degree n are there?

Solution:

There are 2^n different n -tuples of 0s and 1s.

A Boolean function is an assignment of 0 or 1 to each of these 2^n different n -tuples.

Therefore, there are 2^{2^n} different Boolean functions.

24 Nov 2015 CS 320 11

Boolean Identities

There are useful identities of Boolean expressions that can help us to transform an expression A into an equivalent expression B (see Table 5 on page 815 [6th edition: page 753] in the textbook).

24 Nov 2015 CS 320 12

$$\overline{\overline{x}} = x, \text{ law of double complement}$$

$$x+x = x, \text{ idempotent laws}$$

$$x \cdot x = x$$

$$x+0 = x, \text{ identity laws}$$

$$x \cdot 1 = x$$

$$x+1 = 1, \text{ domination laws}$$

$$x \cdot 0 = 0$$

$$x+y = y+x, \text{ commutative laws}$$

$$x \cdot y = y \cdot x$$

24 Nov 2015 CS 320 13

$$x+(y+z) = (x+y)+z, \text{ associative laws}$$

$$x \cdot (y \cdot z) = (x \cdot y) \cdot z$$

$$x+yz = (x+y)(x+z), \text{ distributive laws}$$

$$x \cdot (y+z) = (x \cdot y) + (x \cdot z)$$

$$\overline{(xy)} = \overline{x} + \overline{y}, \text{ De Morgan's laws}$$

$$\overline{(x+y)} = \overline{x} \cdot \overline{y}$$

$$x+xy = x, \text{ Absorption laws}$$

$$x(x+y) = x$$

$$x+\overline{x} = 1, \text{ unit property}$$

$$x\overline{x} = 0, \text{ zero property}$$

24 Nov 2015 CS 320 14

Duality

We can derive additional identities with the help of the **dual** of a Boolean expression.

The dual of a Boolean expression is obtained by interchanging Boolean sums and Boolean products and interchanging 0s and 1s.

24 Nov 2015 CS 320 15

Duality

Examples:

The dual of $x(y+z)$ is $x+yz$.

The dual of $\overline{x} \cdot 1 + (\overline{y}+z)$ is $(\overline{x}+0)((\overline{y})z)$.

The dual is essentially the complement, but with any variable x replaced by \overline{x} . (exercise 29, p. 881)

The **dual of a Boolean function F** represented by a Boolean expression is the function represented by the dual of this expression.

This dual function, denoted by F^d , **does not depend** on the particular Boolean expression used to represent F . (exercise 30, page 881 [6th ed. p.756])

24 Nov 2015 CS 320 16

Duality

Therefore, an identity between functions represented by Boolean expressions **remains valid** when the duals of both sides of the identity are taken.

We can use this fact, called the **duality principle**, to derive new identities.

For example, consider the absorption law $x(x+y) = x$.

By taking the duals of both sides of this identity, we obtain the equation $x + xy = x$, which is also an identity (and also called an absorption law).

24 Nov 2015 CS 320 17

Definition of a Boolean Algebra

All the properties of Boolean functions and expressions that we have discovered also apply to **other mathematical structures** such as propositions and sets and the operations defined on them.

If we can show that a particular structure is a Boolean algebra, then we know that all results established about Boolean algebras apply to this structure.

For this purpose, we need an **abstract definition** of a Boolean algebra.

24 Nov 2015 CS 320 18

Definition of a Boolean Algebra

Definition: A Boolean algebra is a set B with two binary operations \vee and \wedge , elements 0 and 1 , and a unary operation $-$ such that the following properties hold for all x, y , and z in B :

$x \vee 0 = x$ and $x \wedge 1 = x$ (identity laws)
 $x \vee \bar{x} = 1$ and $x \wedge \bar{x} = 0$ (domination laws)
 $(x \vee y) \vee z = x \vee (y \vee z)$ and $(x \wedge y) \wedge z = x \wedge (y \wedge z)$ (associative laws)
 $x \vee y = y \vee x$ and $x \wedge y = y \wedge x$ (commutative laws)
 $x \vee (y \wedge z) = (x \vee y) \wedge (x \vee z)$ and $x \wedge (y \vee z) = (x \wedge y) \vee (x \wedge z)$ (distributive laws)

24 Nov 2015 CS 320 19

Boolean Algebras


Examples of Boolean Algebras are:

1. The algebra of all subsets of a set U , with $+ = \cup, \cdot = \cap, - = \text{complement}, 0 = \emptyset, 1 = U$.
2. The algebra of propositions with symbols p_1, p_2, \dots, p_n , with $+ = \vee, \cdot = \wedge, - = \neg, 0 = F, 1 = T$.
3. If B_1, \dots, B_n are Boolean Algebras, so is $B_1 \times \dots \times B_n$, with operations defined coordinate-wise.


24 Nov 2015 CS 320 20

Logic Gates

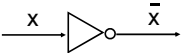
Electronic circuits consist of so-called gates. There are three basic types of gates.
 In each case the input is a Boolean expression and the output is another Boolean expression.



inverter

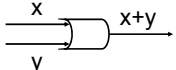

OR gate

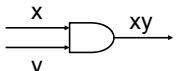


AND gate

24 Nov 2015 CS 320 21

Logic Gates

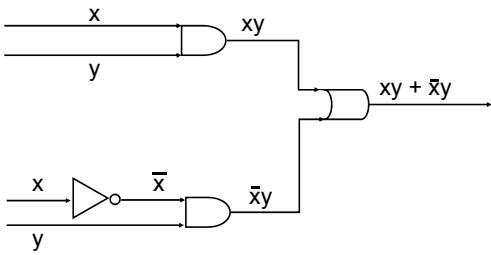Example: How can we build a circuit that computes the function $xy + \bar{x}y$?



24 Nov 2015 CS 320 22

Multi switch light circuit

Suppose we want a circuit for a light controlled by two switches, where changing the state of either switch changes the state of the light (on or off).
 If we let x and y be the states of the switches (0 or 1) then the boolean expression $xy + \bar{x}\bar{y}$ ($- = \text{complement}$) will do the job.

24 Nov 2015 CS 320 23

Multi switch light circuit

This is because if both x and y are “on” (1) or “off” (0) $xy + \bar{x}\bar{y}$ will be 1, and otherwise will be 0.
 We can generalize this method. For three switches the Boolean expression $xyz + x\bar{y}z + \bar{x}yz + \bar{x}\bar{y}z$ will work.
 Can you draw circuits implementing these expressions? (see pp. 825, 826 [6th ed. pp. 763, 764])

24 Nov 2015 CS 320 24

Adding binary integers

If we add two one bit integers x and y we get a sum for that bit position plus a carry bit.

If we don't consider a carry bit from a lower bit addition we get what's called a half adder.

If we do consider an input carry bit we have a full adder. (see p. 827, 6th ed.765)

24 Nov 2015

CS 320

25

Half Adder

Given input bits x and y , the result bit will be $x+y$ unless both x and y are 1, in which case the result is 0.

This means that we can express the result bit as $(x+y)\overline{(xy)}$, or $(x+y)(\overline{x} + \overline{y})$.

The carry bit will be xy (we carry if both x and y are 1)

24 Nov 2015

CS 320

26

Full Adder

If we add a carry bit c_0 from the previous order bit sum our result for this bit would be 1 if one or three of c_0 , x , y are 1, and 0 otherwise.

This means

$xyz_0 + x\overline{y}z_0 + \overline{x}yz_0 + \overline{x}\overline{y}z_0$ would work, with carry bit

$xyz_0 + x\overline{y}z_0 + x\overline{y}z_0 + \overline{x}yz_0$

See p. 827 to check your implementation.

24 Nov 2015

CS 320

27